

# **ECE 444 – Design Project**

## **Temperature Stabilized Ring Oscillator using a Band-gap Reference Voltage Source**

January 20, 2021

**Introduction:** The output frequency of a CMOS ring oscillator is strongly dependent on both the operating temperature and the supply voltage. The frequency increases with increasing supply voltage, and increases with decreasing temperature.

**Part A.** Design a ring oscillator, using the 65nm CMOS process, that has a nominal oscillation frequency of 3 GHz at a temperature of 27°C and supply voltage of  $\sim 1$  V. Simulate the oscillation frequency as a function of temperature (0° to 100° C) and supply voltage (0.8 - 1.4 V). Determine the required supply voltage as a function of temperature needed to stabilize the oscillation frequency at 3 GHz as the temperature is varied between 0° and 100° C

**Part B.** Design a band-gap reference circuit, using the 350nm process, to generate the ring oscillator supply voltage as a function of temperature determined in Part A. The operational amplifier used in the band-gap reference circuit should be biased using a boot-strapped bias circuit. The band-gap reference circuit should compensate the ring oscillator so that the oscillation frequency remains close to 3 GHz as the temperature is varied between 0° and 100° C, and the supply voltage to the band-gap reference circuit is varied between 3.1 and 3.5 V.

A preliminary report describing the results from Part A will be due mid-semester. A final project report describing the design for Part B will be due during final's week.

Designs with minimal variation in the output frequency as a function of the supply voltage and temperature will be considered superior.

### **Specification:**

1. Nominal oscillation frequency: 3 GHz
2. Input voltage: 3.1 – 3.5 V (single rail)
3. Temperature: 0° to 100°C
4. Variation in output frequency: minimal